



# **Khulna University of Engineering & Technology**

## **Department of Electronics and Communication Engineering**

### **Proposal of Analog Electronics II Laboratory (ECE 2102)**

|                             |             |
|-----------------------------|-------------|
| <b>Group: B - 6</b>         |             |
| <b>Name:</b>                | <b>Roll</b> |
| Khondoker Khalid Hasan Kaif | 2309056     |
| Tasfia Tohura               | 2309057     |
| Yasir Arafat Siju           | 2309058     |
| Sabikunnahar Sabira         | 2309059     |
| Shithi Hazra                | 2309060     |

**Signature and Name of the Supervisor**

## **1. Title:**

Design and Implementation of an Op-Amp Based Function Generator for Square, Triangle and Sine Wave Generation.

## **2. Background and Motivation:**

A function generator is an essential electronic instrument used in laboratories, communication systems, and circuit testing applications for producing periodic waveforms such as square, triangle, and sine waves. These waveforms are widely used in signal processing, analog circuit analysis, digital electronics testing, and educational demonstrations. Understanding waveform generation techniques is fundamental for Electronics and Communication Engineering students because it develops practical knowledge of oscillators, amplifiers, and feedback systems.

Operational Amplifiers (Op-Amps) are among the most versatile components in analog electronics. By using Op-Amp based comparator, integrator, and waveform shaping circuits, different periodic signals can be generated efficiently with low-cost components. In this project, the LM741 Op-Amp is used to generate square, triangle, and sine waves within a single integrated circuit system. The square wave is generated using a Schmitt trigger oscillator, the triangle wave is obtained through integration of the square wave, and the sine wave is produced by shaping the triangle waveform using diode-based nonlinear circuitry.

The motivation of this project is to gain hands-on experience in analog circuit design, waveform generation, and practical implementation of theoretical concepts learned in electronic circuit courses. The project also aims to develop a low-cost and educationally valuable laboratory instrument using easily available electronic components.

## **3. Objectives:**

1. To design and implement a square wave generator using LM741 Op-Amp circuitry.
2. To generate a triangle waveform using an Op-Amp integrator circuit.
3. To convert the triangle waveform into a sine wave using a waveform shaping network.
4. To study the working principles of oscillators, comparators, and integrators.
5. To analyze the frequency, amplitude, and stability of generated waveforms.
6. To verify waveform outputs using oscilloscope simulation in Proteus and practical hardware implementation.
7. To develop a compact and low-cost multi-waveform function generator suitable for laboratory applications.
8. To improve practical knowledge of analog electronics and signal generation techniques.

#### 4. Conflicting Requirements:

One of the major conflicting requirements of this project is maintaining waveform accuracy while keeping the circuit simple and cost-effective. The LM741 Op-Amp has limitations such as finite slew rate and bandwidth, which affect waveform quality at higher frequencies. Producing a pure sine wave from a triangle wave requires precise diode shaping and component matching, which conflicts with the goal of minimizing circuit complexity and cost.

Another challenge is achieving frequency stability while allowing adjustable frequency operation. Changing resistor or capacitor values to vary frequency may influence waveform amplitude and distortion. Additionally, noise sensitivity and power supply fluctuations can affect the stability of all generated waveforms simultaneously. Therefore, the design requires a balance between simplicity, performance, stability, and affordability.

#### 5. Proposed Budget for Implementing the Project:

| Sl.                                             | Item                           | Justification                                                            | Price (BDT) |
|-------------------------------------------------|--------------------------------|--------------------------------------------------------------------------|-------------|
| 1.                                              | LM741 Op-Amp ICs               | Main active component for waveform generation and signal processing      | 80          |
| 2.                                              | Resistors and Capacitors       | Required for RC timing circuits, feedback networks, and waveform shaping | 60          |
| 3.                                              | Diodes (1N4007 / Zener Diodes) | Used for sine wave shaping and voltage stabilization                     | 40          |
| 4.                                              | Breadboard, Wires              | Circuit assembly and hardware implementation                             | 150         |
| <b>Total (BDT):</b>                             |                                |                                                                          | 330         |
| <b>In words:</b> Three Hundred Thirty taka only |                                |                                                                          |             |

#### 6. Work Plan (Week wise plan):

|                      |                                                                                                                                                                                                                                     |
|----------------------|-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| 1 <sup>st</sup> Week | Literature review on function generators and Op-Amp based waveform generation techniques. Study of Schmitt trigger, integrator, and sine shaping circuits. Preparation of circuit diagram and simulation planning in Proteus.       |
| 2 <sup>nd</sup> Week | Simulation and implementation of square wave and triangle wave generation circuits using LM741 Op-Amps. Testing, debugging, and frequency adjustment of the outputs.                                                                |
| 3 <sup>rd</sup> Week | Implementation of sine wave shaping circuit and integration of all waveform outputs into a complete function generator system. Final testing using oscilloscope, result analysis, report preparation, and presentation development. |

## **7. Impact of project on the society, environment and sustainability:**

The proposed function generator has significant educational, technical, and economic importance. In educational institutions, it can serve as a low-cost laboratory instrument for studying analog and digital electronics, helping students understand waveform generation and signal analysis practically. Since commercial function generators are comparatively expensive, this project provides an affordable alternative for academic laboratories and hobbyist applications.

From an environmental perspective, the project uses low-power analog components that consume minimal electrical energy, contributing to energy efficiency. The use of reusable and commonly available electronic components also reduces electronic waste and promotes sustainable engineering practices. Furthermore, the project enhances practical engineering skills, encouraging innovation in low-cost electronic system design.

The knowledge and techniques learned through this project can later be applied in communication systems, medical electronics, industrial automation, instrumentation, and embedded systems, thereby contributing positively to technological advancement and sustainable development.